

# Indian Institute Of Technology

Kharagpur, West Bengal, India



## CS29002 SWITCHING CIRCUITS LABORATORY

---

### LABORATORY REPORT 2

---

Student Name	Roll Number
1. Aman Sharma	20CS30063
2. Deepsikha Behera	20CS10023
3. Umika Agrawal	20CS30056

Group Number: 2

Submission Date : 03/02/2022

# 1 Problem Statement (BCD)

Develop circuits to convert from 4-bit binary to 2-digit BCD.

## Solution

- The input in this is a 4-bit binary code and it needs to be converted to a 2 digit, i.e. 8 bit BCD code.
- As the range of a 4 bit binary code is from 0 to 15, the BCD output would be of the form 000B<sub>4</sub>B<sub>3</sub>B<sub>2</sub>B<sub>1</sub>B<sub>0</sub>
- In this solution, we'll determine the values of B<sub>4</sub>, B<sub>3</sub>, B<sub>2</sub>, B<sub>1</sub> and B<sub>0</sub>.

### 1. Truth Table

The input is a 4-bit binary code, so the input has 16 possible combinations. Hence, the output should have 8-bit, but because the first three bit will all be 0 for all combinations of inputs, the output can be treated as 5-bit BCD code(B<sub>4</sub> B<sub>3</sub> B<sub>2</sub> B<sub>1</sub> B<sub>0</sub>). The conversion of binary code into BCD code as shown as follows:

Decimal	Binary code				BCD Code				
	A	B	C	D	B <sub>4</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	0	1
2	0	0	1	0	0	0	0	1	0
3	0	0	1	1	0	0	0	1	1
4	0	1	0	0	0	0	1	0	0
5	0	1	0	1	0	0	1	0	1
6	0	1	1	0	0	0	1	1	0
7	0	1	1	1	0	0	1	1	1
8	1	0	0	0	0	1	0	0	0
9	1	0	0	1	0	1	0	0	1
10	1	0	1	0	1	0	0	0	0
11	1	0	1	1	1	0	0	0	1
12	1	1	0	0	1	0	0	1	0
13	1	1	0	1	1	0	0	1	1
14	1	1	1	0	1	0	1	0	0
15	1	1	1	1	1	0	1	0	1

## 2. Analysis

- **B<sub>0</sub>**

As B<sub>0</sub> is the 1<sup>st</sup> bit of the ones digit, it would be the same as the first bit of the input.

$$B_0 = D$$

- **B<sub>1</sub>**

From the truth table above, we can write the expression for B<sub>1</sub> as follows:

$$\begin{aligned} B_1 &= \overline{A}B\overline{C}\overline{D} + \overline{A}BCD + \overline{A}B\overline{C}D + A\overline{B}\overline{C}\overline{D} + AB\overline{C}D \\ B_1 &= \overline{A}B\overline{C}(\overline{D} + D) + \overline{A}BC(\overline{D} + D) + AB\overline{C}(\overline{D} + D) \end{aligned}$$

As

$$\begin{aligned} \overline{D} + D &= 1 \\ B_1 &= \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C} \\ B_1 &= AB\overline{C} + \overline{A}C(\overline{B} + B) \end{aligned}$$

$$B_1 = AB\overline{C} + \overline{A}C$$

- **B<sub>2</sub>**

From the truth table above, we can write the expression for Y as follows:

$$\begin{aligned} B_2 &= \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + \overline{A}BCD + AB\overline{C}\overline{D} + AB\overline{C}D \\ B_2 &= \overline{A}B\overline{C}(\overline{D} + D) + \overline{A}BC(\overline{D} + D) + AB\overline{C}(\overline{D} + D) \end{aligned}$$

As

$$\begin{aligned} \overline{D} + D &= 1 \\ B_2 &= \overline{A}B\overline{C} + \overline{A}BC + AB\overline{C} \\ B_2 &= \overline{A}B(\overline{C} + C) + AB\overline{C} \\ B_2 &= \overline{A}B + AB\overline{C} \\ B_2 &= B(\overline{A} + A\overline{C}) \end{aligned}$$

As

$$\begin{aligned} A + B\overline{C} &= (A + B)(A + \overline{C}) \\ B_2 &= B(\overline{A} + A)(\overline{A} + \overline{C}) \\ B_2 &= B(\overline{A} + \overline{C}) \\ B_2 &= \overline{A}B + B\overline{C} \end{aligned}$$

- **B<sub>3</sub>**

From the truth table above, we can write the expression for X as follows:

$$\begin{aligned} B_3 &= A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D \\ B_3 &= A\overline{B}\overline{C}(\overline{D} + D) \end{aligned}$$

As

$$\begin{aligned} \overline{D} + D &= 1 \\ B_3 &= A\overline{B}\overline{C} \end{aligned}$$

- $B_4$

From the truth table above, we can write the expression for W as follows:

$$B_4 = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}CD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + ABC\overline{D} + ABCD$$

$$B_4 = \overline{A}\overline{B}C(\overline{D} + D) + AB\overline{C}(\overline{D} + D) + ABC(\overline{D} + D)$$

As

$$\overline{D} + D = 1$$

$$B_4 = \overline{A}\overline{B}C + AB\overline{C} + ABC$$

$$B_4 = \overline{A}\overline{B}C + AB(\overline{C} + C)$$

$$B_4 = A(\overline{B}C + B)$$

As


$$A + BC = (A + B)(A + C)$$

$$B_4 = A(\overline{B} + B)(B + C)$$

$$B_4 = A(B + C)$$

$$B_4 = AB + AC$$

### 3. Circuit Diagram

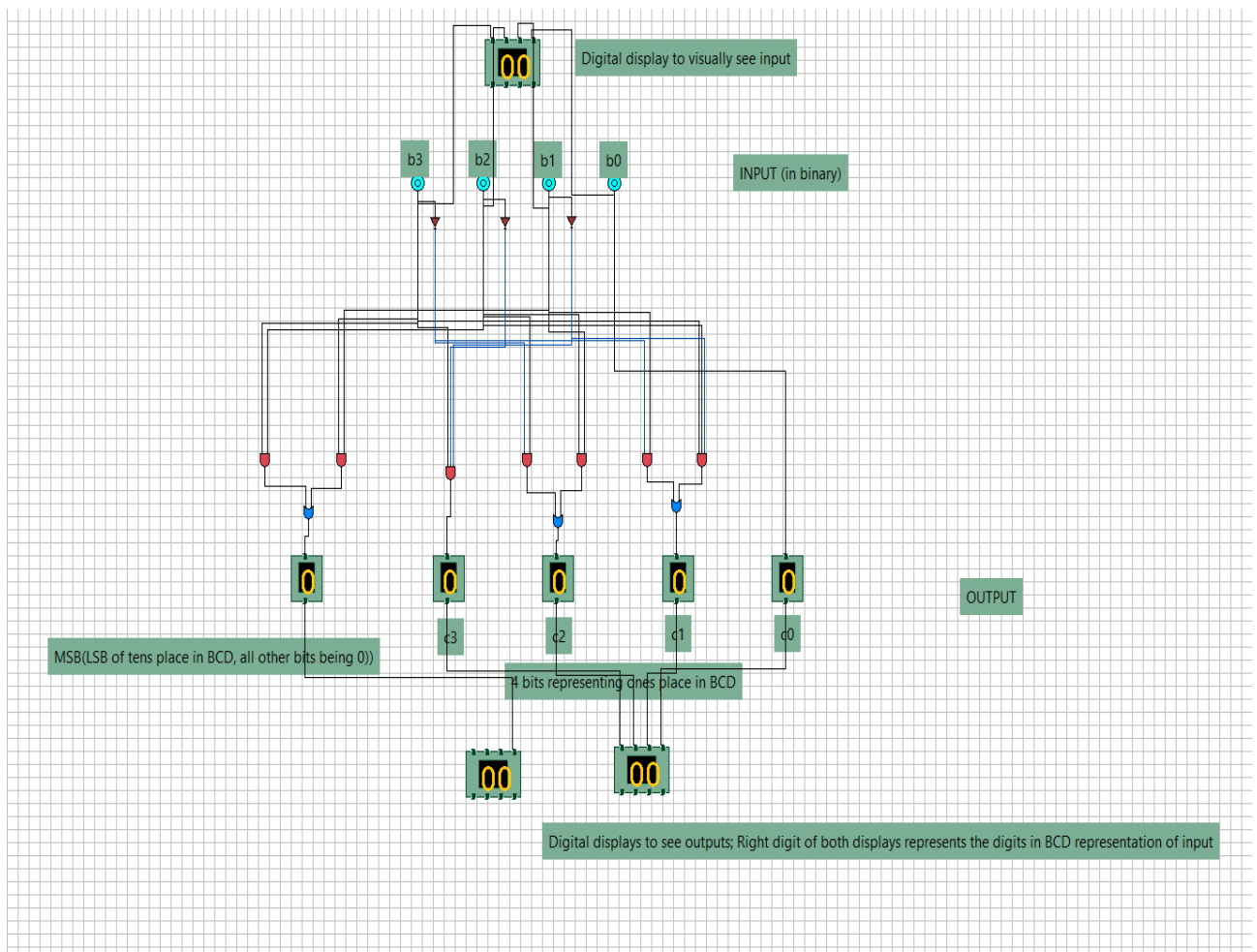

## 2 Problem Statement (Gray)

Develop circuits to convert from 4-bit Gray to 4-bit binary and vice-versa.

### 1. Truth Table

Decimal numbers	Binary code				Gray Code			
	B <sub>1</sub>	B <sub>2</sub>	B <sub>3</sub>	B <sub>4</sub>	G <sub>1</sub>	G <sub>2</sub>	G <sub>3</sub>	G <sub>4</sub>
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	1	1	0
5	0	1	0	1	0	1	1	1
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	0	0
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	1	1	1	1
11	1	0	1	1	1	1	1	0
12	1	1	0	0	1	0	1	0
13	1	1	0	1	1	0	1	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	1	0	0	0

### 2. Binary to Gray:

Theory:


- Gray code is made such that the consecutive numbers differ in just 1 bit.
- The last bit from the right (MSB) is always the same in gray as the binary code.

- The further bits( $n^{\text{th}}$  bit) are obtained by the method that  $n^{\text{th}}$  bit of gray is the XOR of  $n^{\text{th}}$  and  $(n+1)^{\text{th}}$  bit of the binary code.

$$G_i = B_i \text{ for } i=n$$

$$G_i = B_i \text{ XOR } B_{i+1} \text{ for } i \in [0, n-1]$$

**Circuit Diagram:**

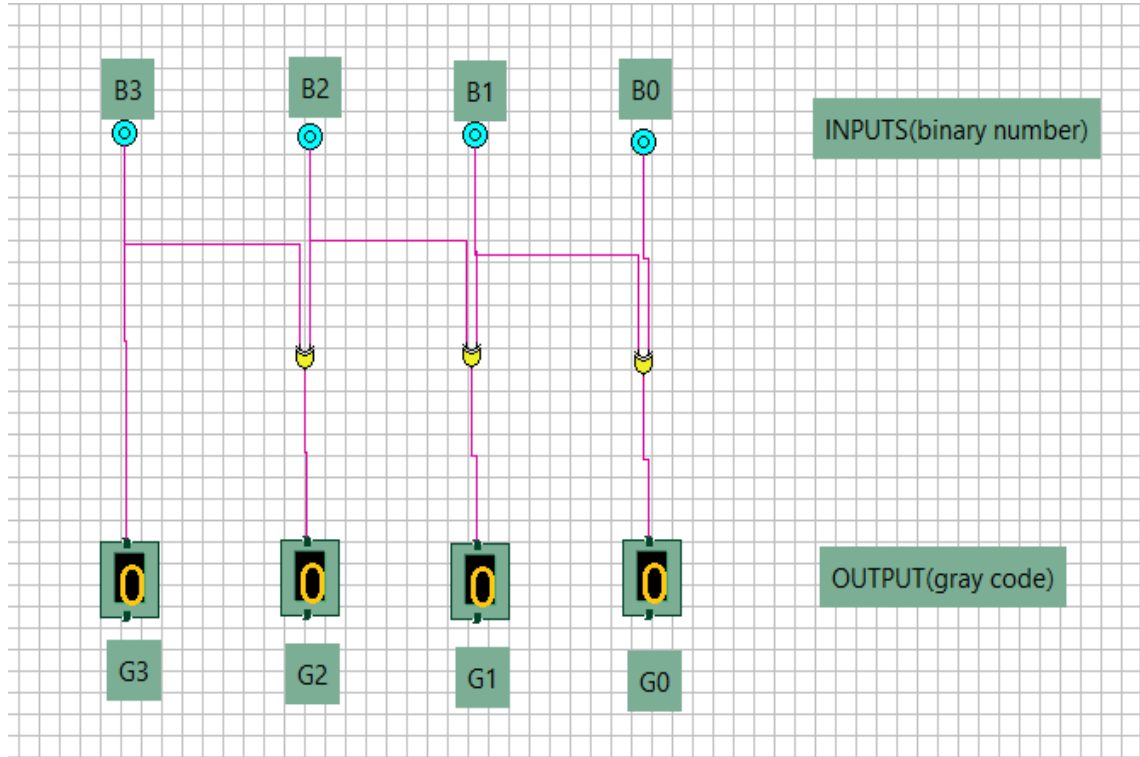

### 3. Gray to Binary:


**Theory:**

- The MSB of the binary number is the same as the MSB of the gray code.
- The  $2^{\text{nd}}$  bit(from the left) of the binary number is the same as the  $1^{\text{st}}$  bit of the binary number if the  $2^{\text{nd}}$  bit of the Gray code is 0. Else, the  $2^{\text{nd}}$  bit is the opposite of the  $1^{\text{st}}$  bit of the binary number.
- The same follows for all the further bits of the binary number( $B_i$  and  $G_i$  are the  $i^{\text{th}}$  bits from the right)

$$B_i = G_i \text{ for } i = n$$

$$B_i = G_i \text{ XOR } B_{i+1} \text{ for } i \in [0, n-1]$$

### Circuit Diagram:

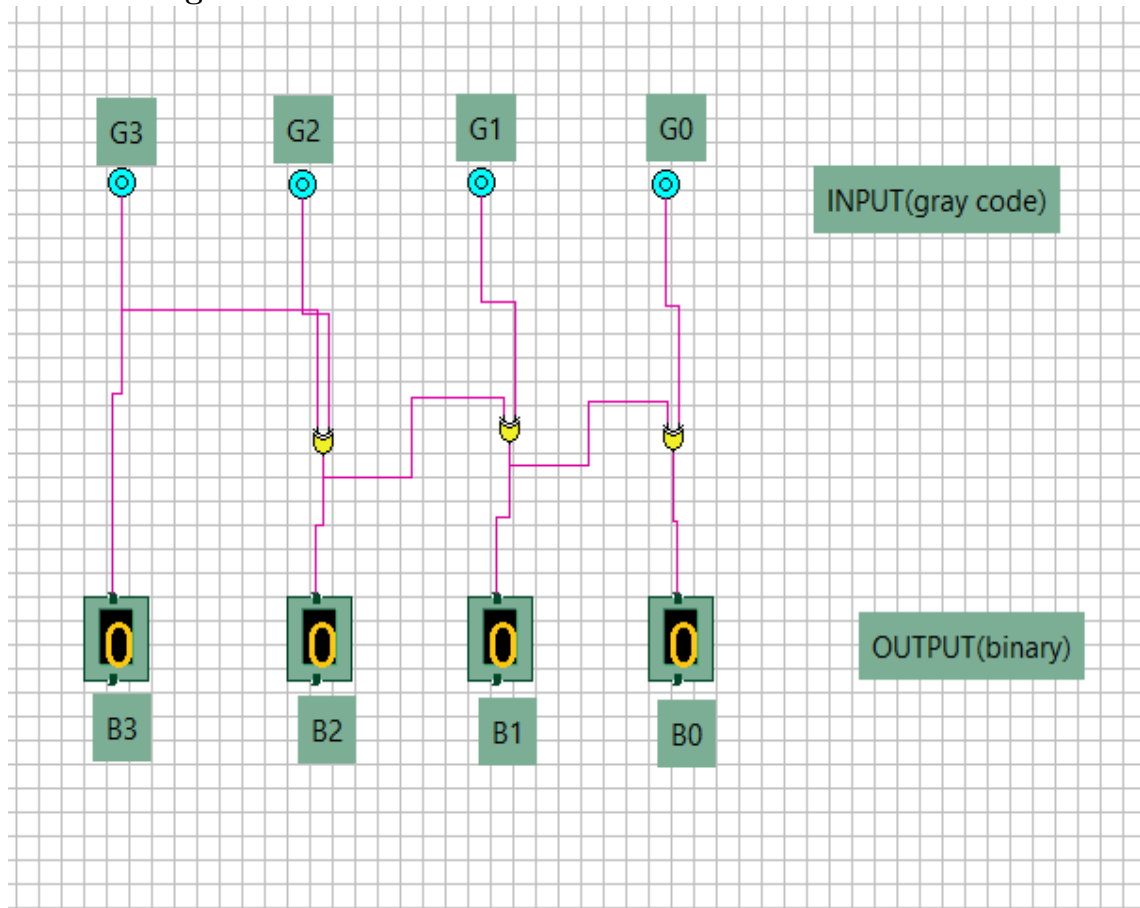

### 3 Problem Statement (Excess-3)

- Develop a half adder for handling two bits.
- Develop a full adder using half adders and any additional logic.
- Develop a ripple carry adder needed for this assignment using full adders.
- Develop circuits to convert from excess-3 to 4-bit binary and vice-versa.

### Solution

#### • Half Adder

A half adder is a logical circuit which finds the sum of two binary digits, and outputs a Sum and a Carry value.


**Truth Table**

Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\begin{aligned}\text{Sum} &= A \text{ XOR } B \\ \text{Carry} &= A \text{ AND } B\end{aligned}$$



## Circuit Diagram

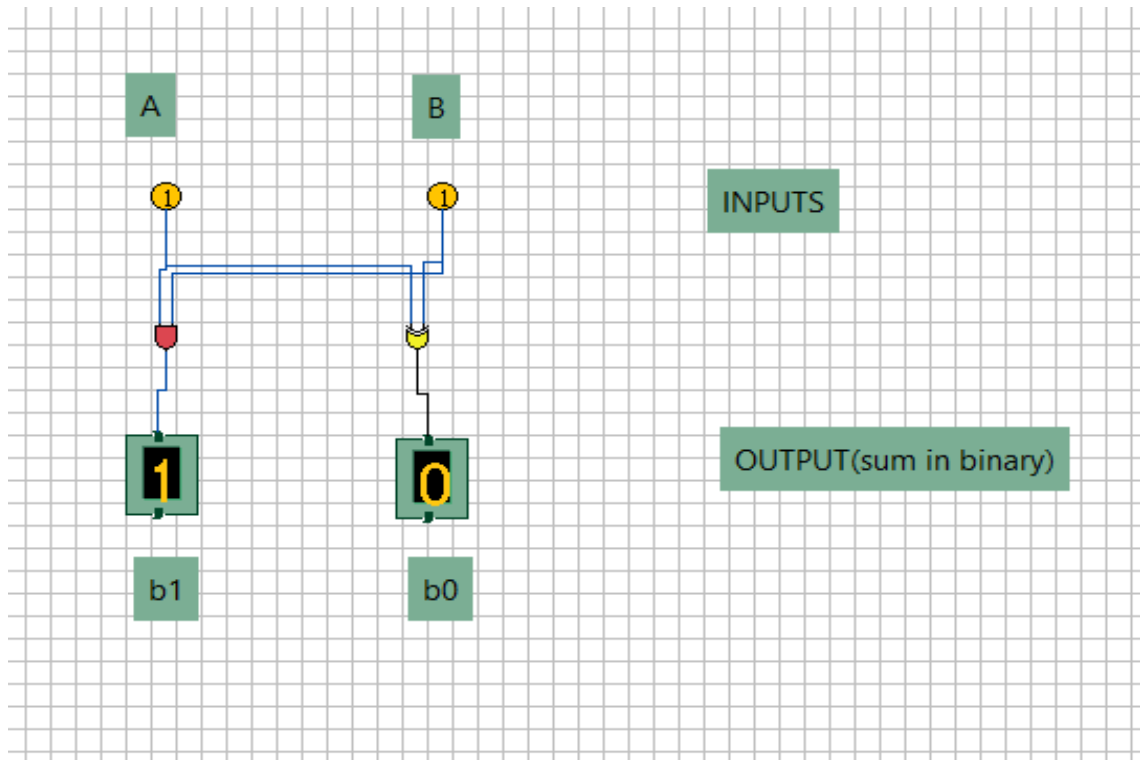

### • Full Adder

A full adder is a logical circuit that finds the sum of three binary digits, and outputs a SUM and a Carry-out(C-OUT) value. The first two inputs are A and B, and the third input is C-IN.

#### Truth Table

Input			Output	
A	B	C(Cin)	Sum	Carry(Cout)
0	0	0	0	0
1	0	0	1	0
0	1	0	1	0
0	0	1	1	0
1	1	0	0	1
1	0	1	0	1
0	1	1	0	1
1	1	1	1	1

Logical Expression for SUM:  

$$= \overline{A}BC\text{-IN} + A\overline{B}C\text{-IN} + AB\overline{C}\text{-IN}$$

$$= C\text{-IN}(\overline{A}B + A\overline{B}) + \overline{C}\text{-IN}(\overline{A}B + A\overline{B})$$


$$= C\text{-IN XOR } (A \text{ XOR } B)$$

Logical Expression for C-OUT:  

$$= \overline{A}BC\text{-IN} + A\overline{B}C\text{-IN} + ABC\text{-IN} + ABC\text{-IN}$$


$$= AB + BC\text{-IN} + AC\text{-IN}$$

### Circuit Diagram

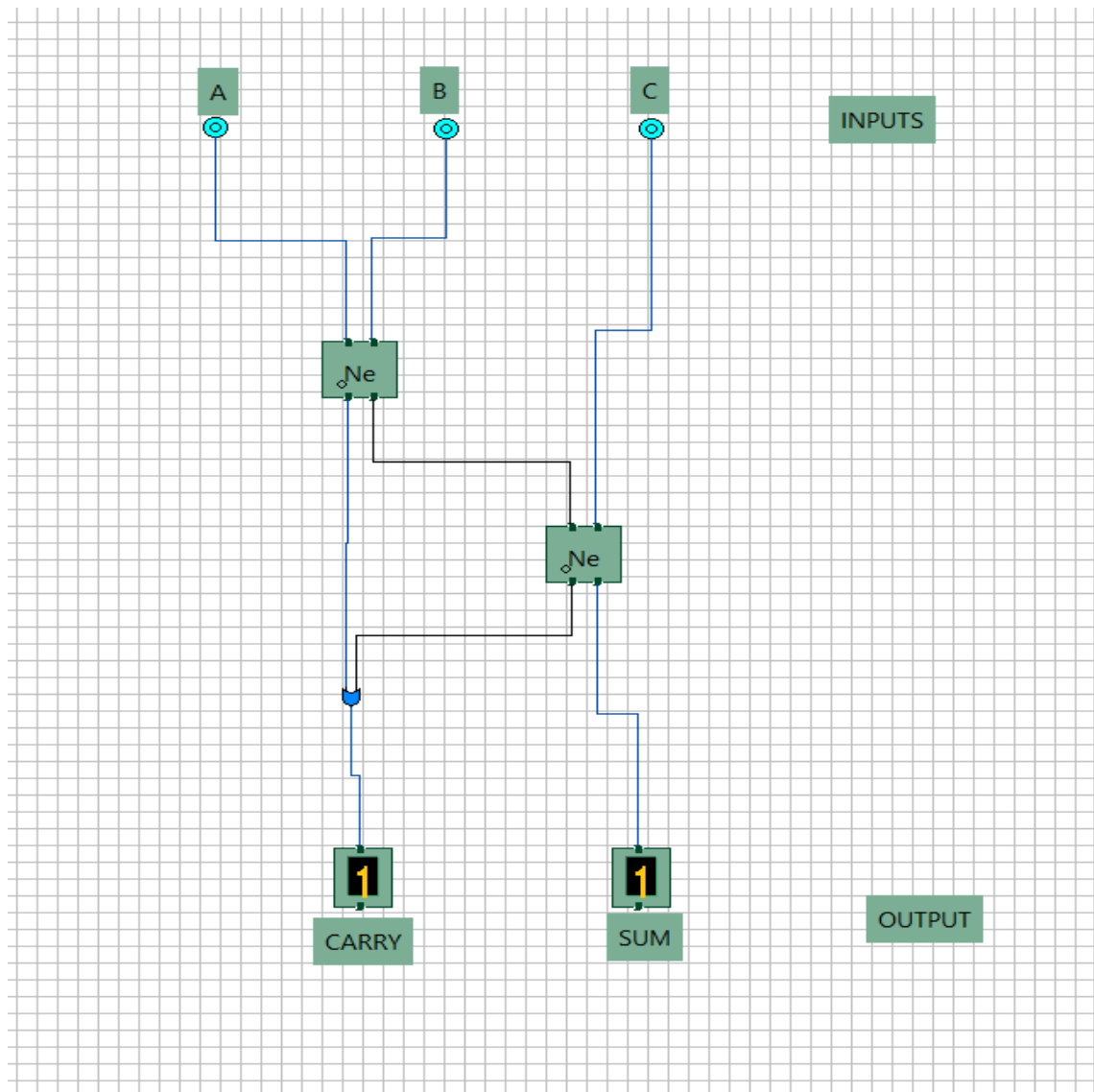
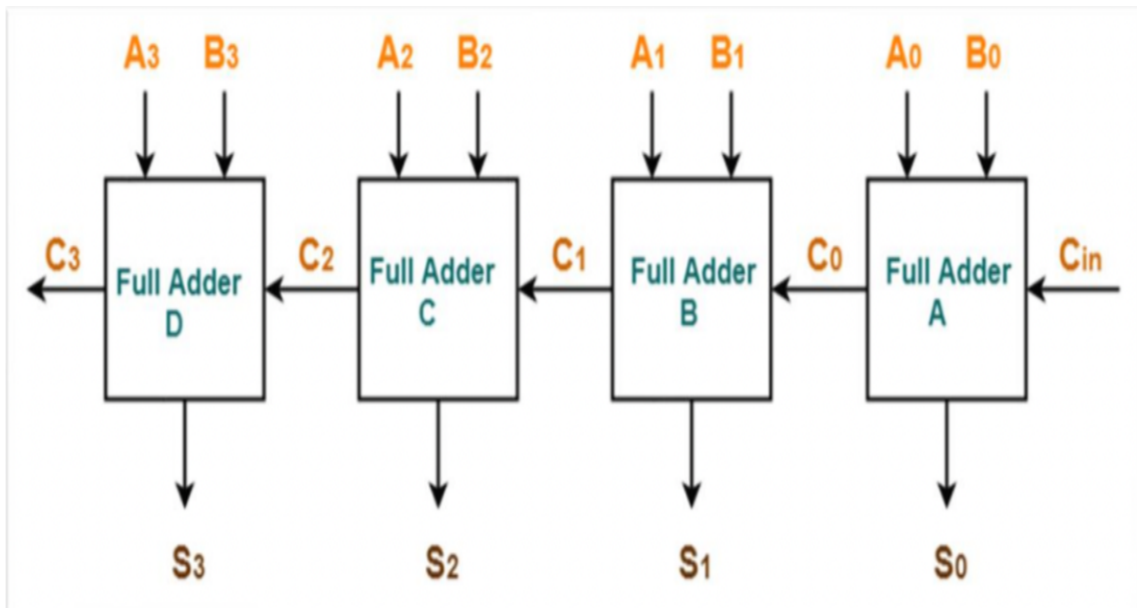
### • Ripple Carry Adder

A ripple carry adder is a logical circuit which finds the sum of two n-bit binary numbers. It is made by using n full adders. Each full adder acts as a single weighted column in a long binary addition.




The minimised expression for each output using k-map is:

- $S_0 = A_0 \oplus B_0 \oplus C_{in}$
- $C_0 = A_0 \cdot B_0 \oplus B_0 \cdot C_{in} \oplus C_{in} \cdot A_0$
- $S_1 = A_1 \oplus B_1 \oplus C_0$
- $C_1 = A_1 \cdot B_1 \oplus B_1 \cdot C_0 \oplus C_0 \cdot A_1$
- $S_2 = A_2 \oplus B_2 \oplus C_1$
- $C_2 = A_2 \cdot B_2 \oplus B_2 \cdot C_1 \oplus C_1 \cdot A_2$
- $S_3 = A_3 \oplus B_3 \oplus C_2$
- $C_3 = A_3 \cdot B_3 \oplus B_3 \cdot C_2 \oplus C_2 \cdot A_3$

However, using full adders we just provide the Carry out of the last adder to the next adder as Carry in. Thus, we get an n-bit adder using n full adders.

## Circuit Diagram

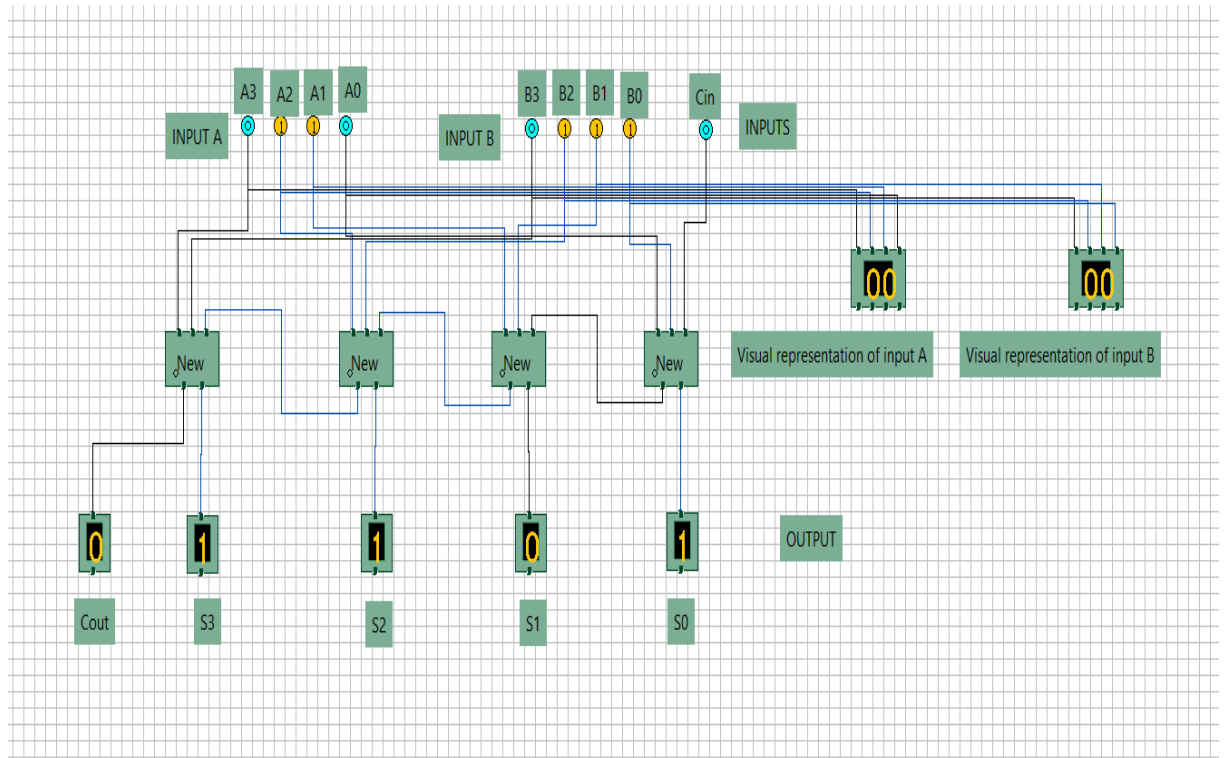


### • Binary to Excess-3 code

In Excess-3 code, each digit of the decimal number is represented by adding 3 to it.

To convert from binary code to excess-3 code:

- Convert Binary to decimal
- Add 3 to every digit
- Find binary representation of each digit
- We can also convert Binary to BCD first, and add 0011 to each digit in the BCD code.


## Circuit Diagram

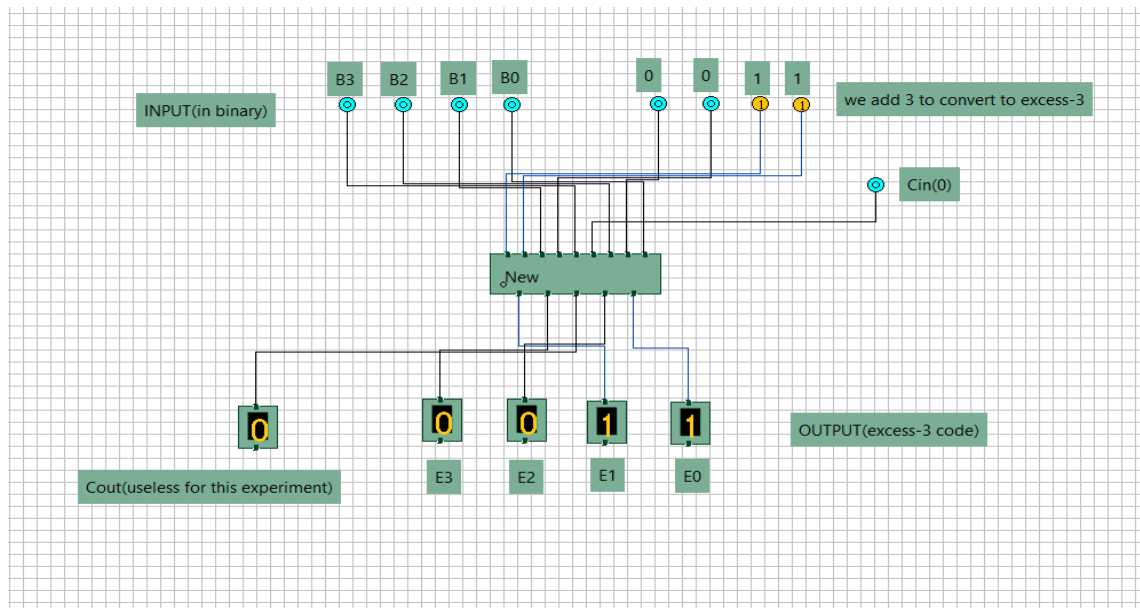

## • Excess-3 to Binary code

- Convert Excess-3 to BCD (by subtracting 0011) from every digit.
- Convert the BCD code to Binary code.

## Circuit Diagram

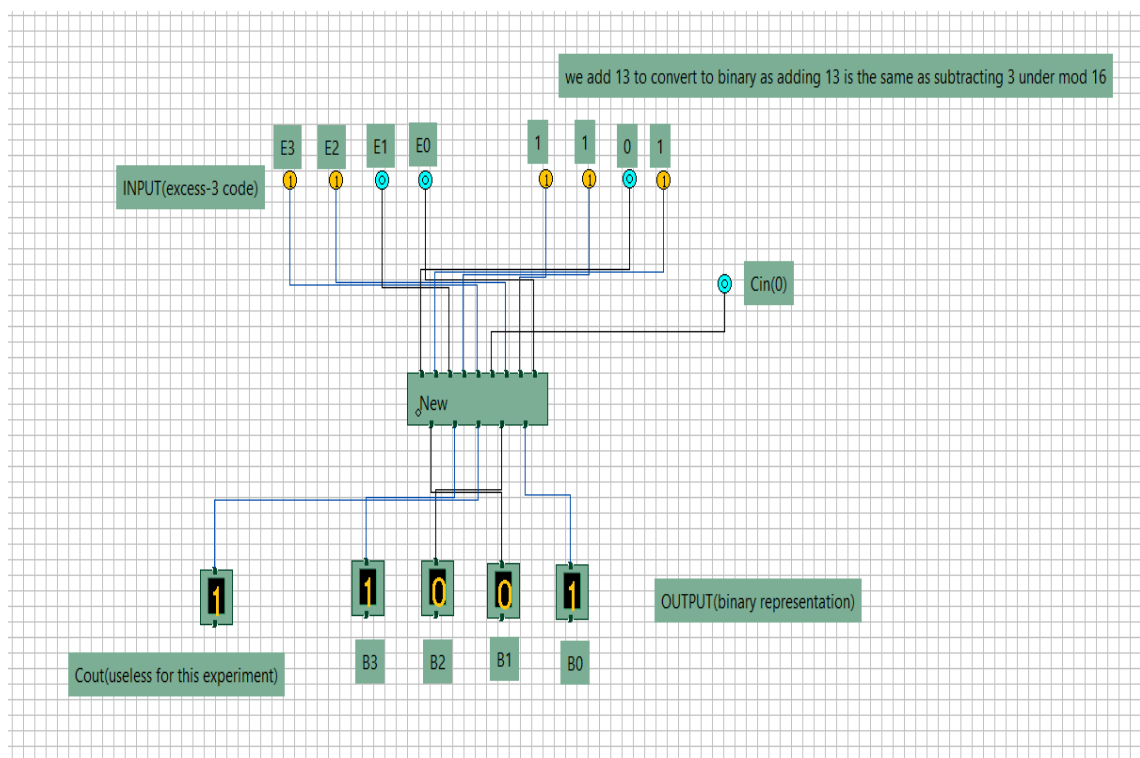

Conversion Table between EXCESS-3 code and binary

EXCESS-3 INPUT				BCD OUTPUT			
E3	E2	E1	E0	B3	B2	B1	B0
0	0	0	0	X	X	X	X
0	0	0	1	X	X	X	X
0	0	1	0	X	X	X	X
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	1
0	1	0	1	0	0	1	0
0	1	1	0	0	0	1	1
0	1	1	1	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	1	1	1
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X